

# Digital Logic Design

## Problem Set #5

Due Date: 1400/9/1



1. Design a full adder module with data inputs  $A$  and  $B$ , carry input  $C_{in}$ , sum output  $S$ , and carry output  $C_{out}$  using two 4-to-1 multiplexers. (20 points)
2. Design a logic circuit that multiplies two 3-bit numbers,  $(a_2a_1a_0)_2$  and  $(b_2b_1b_0)_2$ , using only NAND gates. The product should be a 6-bit number  $(p_5p_4p_3p_2p_1p_0)_2$  (30 points)
3. Design a 16-to-4 priority encoder by cascading enough 74148 IC's. (25 points)
4. Design a 16bit ALU by cascading enough 74181 ALUs. Feel free to use any component you need. (hint: you may need a 74182 IC). (25 points)

*Good Luck!*

*Mosayebi*

*Do not hesitate to ask your question*

*Via eeXBee@gmail.com*