

Digital Logic Design


Problem Set #9

Due Date: 1400/9/30




1- Given the synchronous circuit below: (50 points)

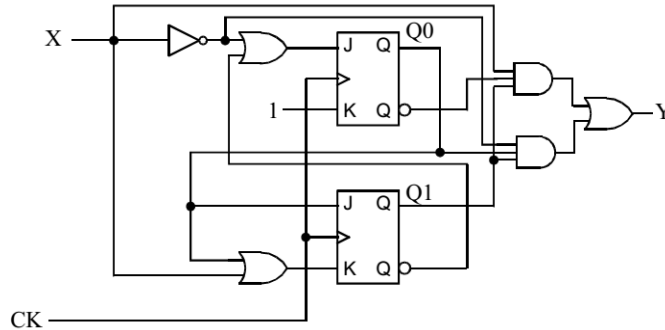- Find the state diagram
- Find the state and output equations



2- Given the synchronous circuit below: (50 points)

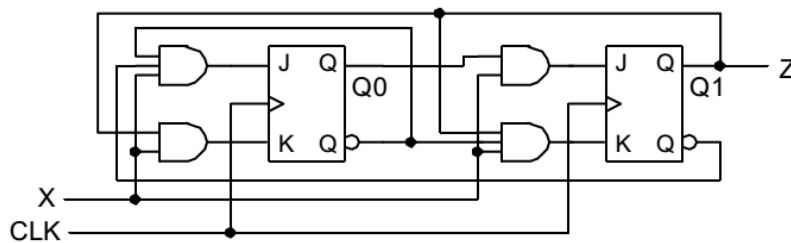- Find the state diagram
- Find the state and output equations



Good Luck!

Mosayebi

Do not hesitate to ask your question
Via eeXBee@gmail.com